

Total No. of Questions : 4]

SEAT No. :

P-5402

[Total No. of Pages : 2

[6186]-528

S.E. (Information Technology) (In Sem.)

**LOGIC DESIGN & COMPUTER ORGANIZATION**  
**(2019 Pattern) (Semester - III) (214442)**

Time : 1 Hour]

[Max. Marks : 30

Instructions to the candidates :

- 1) Answer Q.1 or Q.2 and Q.3 or Q.4.
- 2) Neat diagrams must be drawn wherever necessary.
- 3) Figures to the right side indicate full marks.
- 4) Assume Suitable data if necessary.

**UNIT - 1**

**Q1) a) Do the following :** [5]

- i)  $(735.25)_{10} = (?)_{16}$
  - ii)  $(101011.111011)_2 = (?)_8 = (?)_{10}$
  - iii) Convert 1110 gray to binary and convert binary 1011 to gray
- b) Simplify and implement following function using k-map [5]
- $f(A,B,C,D) = \sum m(0,2,5,6,7,8,10,13,14,15)$
- c) Explain the working of a 2-input CMOS NAND gate with suitable figures? [5]

OR

**Q2) a) Represent the decimal numbers :** [5]

- i) 396 in : 1 .BCD 2.Excess -3 code.
  - ii) Represent +40 and -40 decimal numbers using 2's complement.
- b) Add the binary numbers
- i) 1011 and 1100
  - ii) 0101 and 1111
- c) What is Logic family? Explain any four characteristics of digital lcs.[5]

P.T.O.

## UNIT - 2

- Q3)** a) Design and explain full subtractor using IC 74138? [5]  
b) Explain and Design Full Adder using Half Adder? [5]  
c) Implement Full Adder using demultiplexer? [5]

OR

- Q4)** a) Implement the following Boolean function using single 8 : 1 multiplexer  
 $f(A,B,C,D) = \sum m(1,4,6,9,13)$  [5]  
b) Explain BCD to excess-3 code converter with logic diagram? [5]  
c) Add  $(83)_{10}$  and  $(34)_{10}$  in BCD? [5]

